

Carry-Skip Adder

Carry-LookAhead Adder

Review

Chaitanya Tejaswi
(214102408)

Indian Institute of Technology, Guwahati
April 15, 2022




Overview

- 1 Ideas
- 2 Carry-Ripple Adder
- 3 Carry-Skip Adder
- 4 Carry-LookAhead Adder
- 5 References

Ideas

 - 1 Carry-Propagate Adders: C_{in} influences all subsequent bits. C_{out} is "Majority Gate".



Example of carry propagation

$$\begin{aligned}
 S &= \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC \\
 &= (A \oplus B) \oplus C = P \oplus C \\
 C_{out} &= AB + AC + BC \\
 &= AB + C(A + B) \\
 &= \overline{\overline{AB} + \overline{C}(\overline{A} + \overline{B})} \\
 &= \text{MAJ}(A, B, C)
 \end{aligned}$$

$$\begin{aligned}
 G &= AB \\
 P &= A \oplus B \\
 K &= \overline{AB} \\
 &= \overline{A + B} \\
 &\text{full adder}
 \end{aligned}$$

- 2 Propagate, Generate or Kill (PGK)

A group of bits:

generates a carry if its C_{out} is true independent of the C_{in}

propagates a carry if its C_{out} is true when there is a C_{in}


kills a carry if its C_{out} is false independent of the C_{in}

Ideas

3 Abstracting ckt implementation using Group PGK signals

For a full adder:
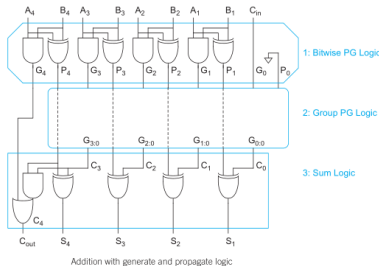
$$\begin{aligned}
 G &= AB \\
 P &= A \oplus B \\
 K &= \overline{AB} \\
 &= \overline{A + B}
 \end{aligned}$$



$$G_{i:j} = G_{i:k} + P_{i:k} \cdot G_{k-1:j}$$

$$P_{i:j} = P_{i:k} \cdot P_{k-1:j}$$

where

$$G_{i:i} \equiv G_i = A_i \cdot B_i$$

$$P_{i:i} \equiv P_i = A_i \oplus B_i$$

Sum:

$$S_i = P_i \oplus G_{i-1:0}$$

Carry-Ripple Adder

C_{out} of previous stage is connected to C_{in} of next stage.

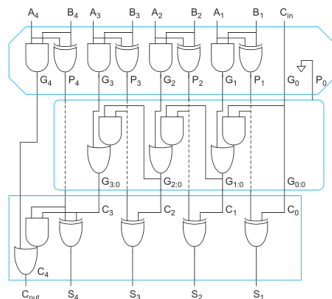


FIGURE 11.14 4-bit carry-ripple adder using PG logic

where

$$\begin{aligned} C_i &= A_i B_i + (A_i + B_i) C_{i-1} & G_{i:0} &= G_i + P_i \cdot G_{i-1:0} \\ &= A_i B_i + (A_i \oplus B_i) C_{i-1} \\ &= G_i + P_i C_{i-1} \end{aligned}$$

 


FIGURE 11.15 Carry-ripple adder group PG network


$$t_{\text{ripple}} = t_{pg} + (N - 1) t_{AO} + t_{xor}$$

Figure: Carry-Ripple Adder: Block Diagram, CriticalPath Delay (1)

Carry-Skip Adder

Computes group propagation-delay (t_p) for each Carry chain, and uses this to skip long carry ripples.

 Skip MUX selects group C_{in} if $P = 1$, C_{out} if $P = 0$.



$$t_{\text{skip}} = t_{pg} + 2(n-1)t_{AO} + (k-1)t_{\text{mux}} + t_{\text{xor}}$$

Figure: Carry-Skip Adder: Block Diagram, CriticalPath Delay (1)

Carry-Skip Adder

Pro: Low/High Weights


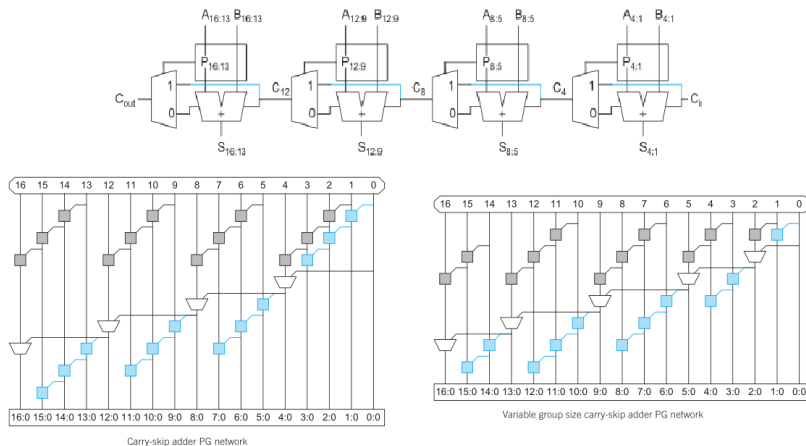


Figure: Carry-Skip Adder: Propagate/Generate (1)

Carry-LookAhead Adder

 Computes group propagation & generation delays (t_p , t_g) for each Carry chain, and uses this to skip long carry ripples.
Skip MUX selects group C_{in} if $P = 1$, C_{out} if $P = 0$.



$$t_{cla} = t_{pg} + t_{pg(n)} + [(n-1) + (k-1)] t_{AO} + t_{xor}$$

Carry-LookAhead Adder

Pro: Parallelization

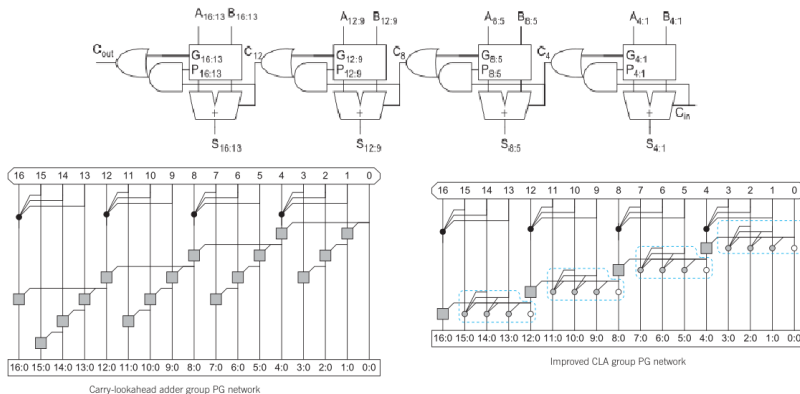


Figure: Carry-LookAhead Adder: Propagate/Generate (1)

References

- [1] N. Weste and D. Harris, *CMOS VLSI Design: A Circuits and Systems Perspective*. USA: Addison-Wesley Publishing Company, 4th ed., 2010.

Thank You!